

Homework2 partA

1.1)

1.1

$V_{in} > V_{th} (5.5V)$

V_{out} from high to low


$V^+ = -V^- = 10V$

$V_{out} = V_{in} \frac{R_2}{R_1 + R_2} = 10 \frac{3.3}{3.3 + 2.7} = 5.5V$

$V_{th} = 5.5V$

$R_2 = 3.3\Omega$ $R_1 = 2.7\Omega$

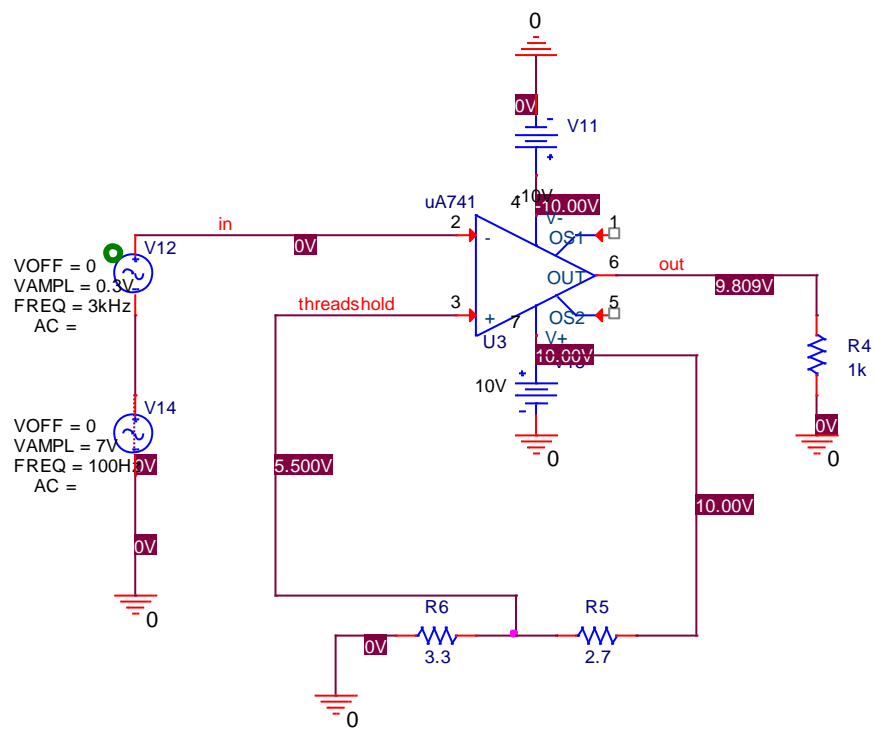
1.2 The engineer is right. Noisy input can cause many closely-spaced output transitions as it passes through threshold. But if the threshold connect to a constant voltage source, the op-amp output goes into negative saturation whenever $V_{in} > V_{th}$. The buffer





$$V_{th} = 5.5V \quad V_{th \text{ high}} = 5.5V \quad (5.5) \dots = \frac{R_1 R_2}{R_1 + R_2} \quad R_2 = 3.3\Omega \quad R_1 = 2.7\Omega$$

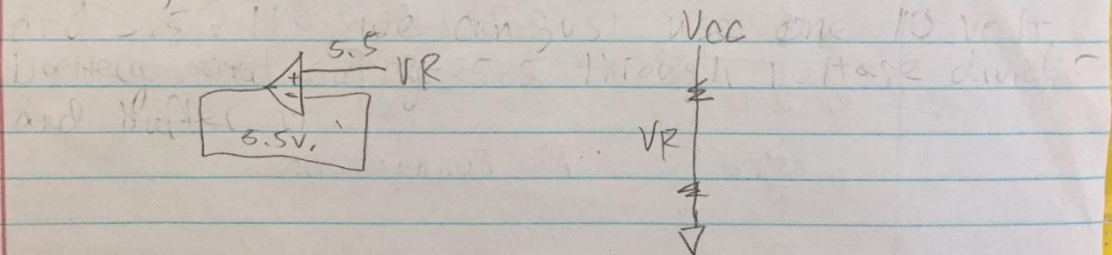
1.2 The engineer is right, Noisy input can cause many closely-spaced output transitions as it passes through threshold. But if the threshold connect to a constant voltage source, the op-amp output goes into negative saturation whenever $V_{in} > V_{th}$. The buffer will create constant voltage source when connect to a voltage divider.




$$1.3 \quad V_R = V_{in} \frac{R_2}{R_1 + R_2} = \frac{9(3.3)}{3.3 + R_1} = 3.89V \quad R_1 = 4.47\Omega \quad R_2 = 3.3\Omega$$



$$V_{2H} = V_{ref} = 4.1V$$

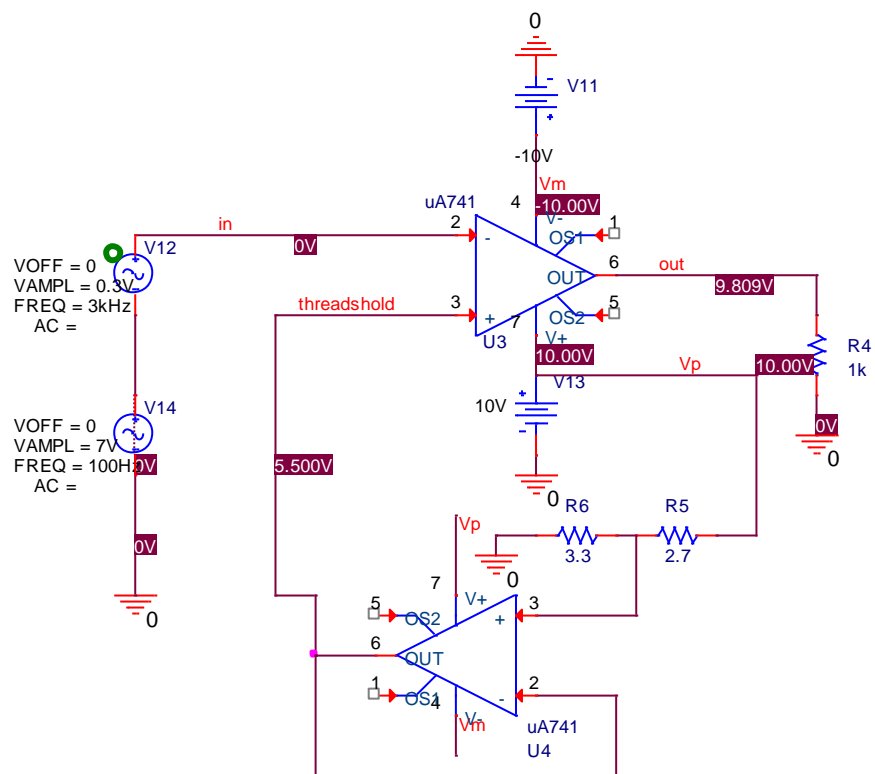
The noise peak-to-peak amplitude is $0.9V$. In order to avoid "ringing" we have to take $\Delta > 0.9V$.



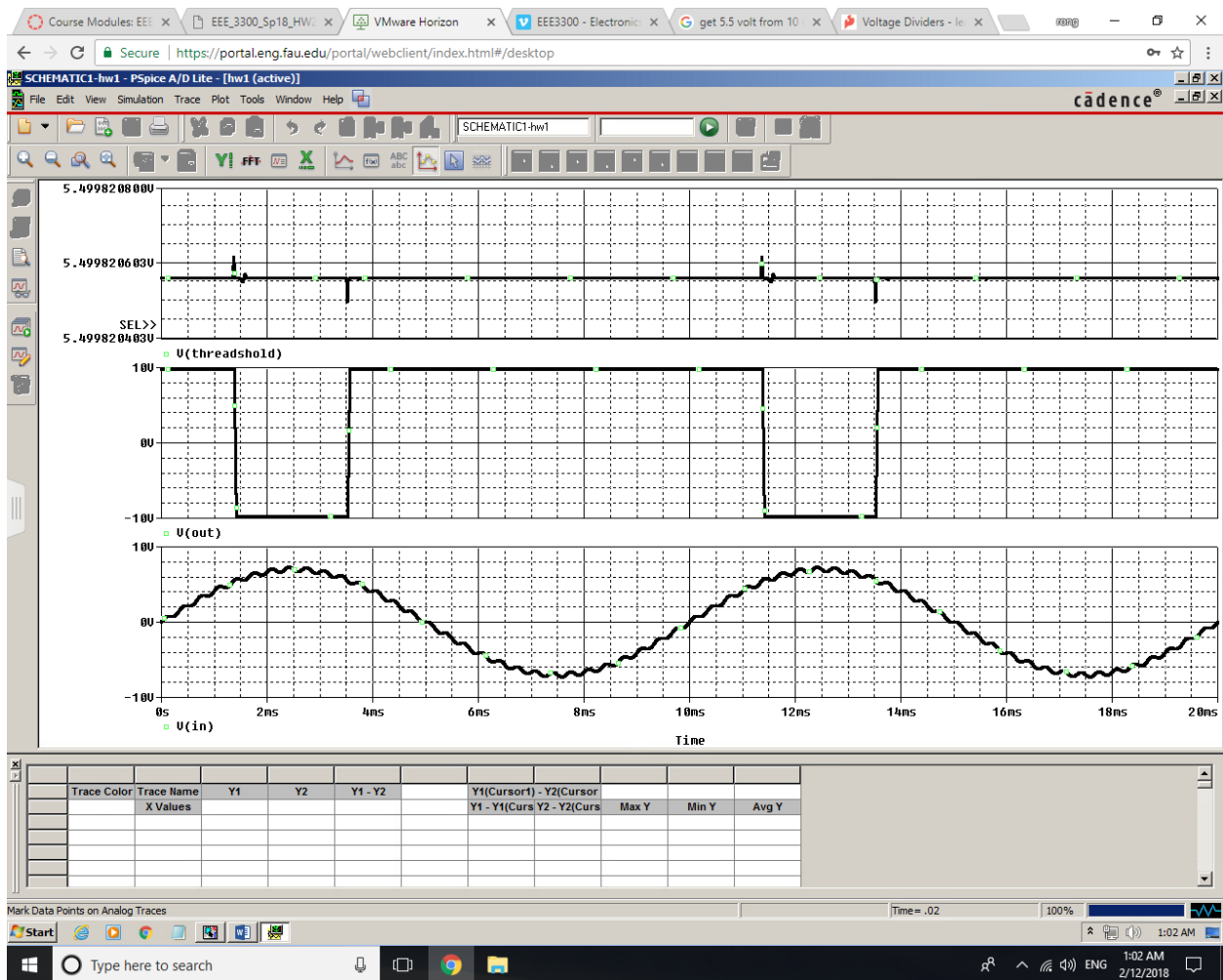


1.3)

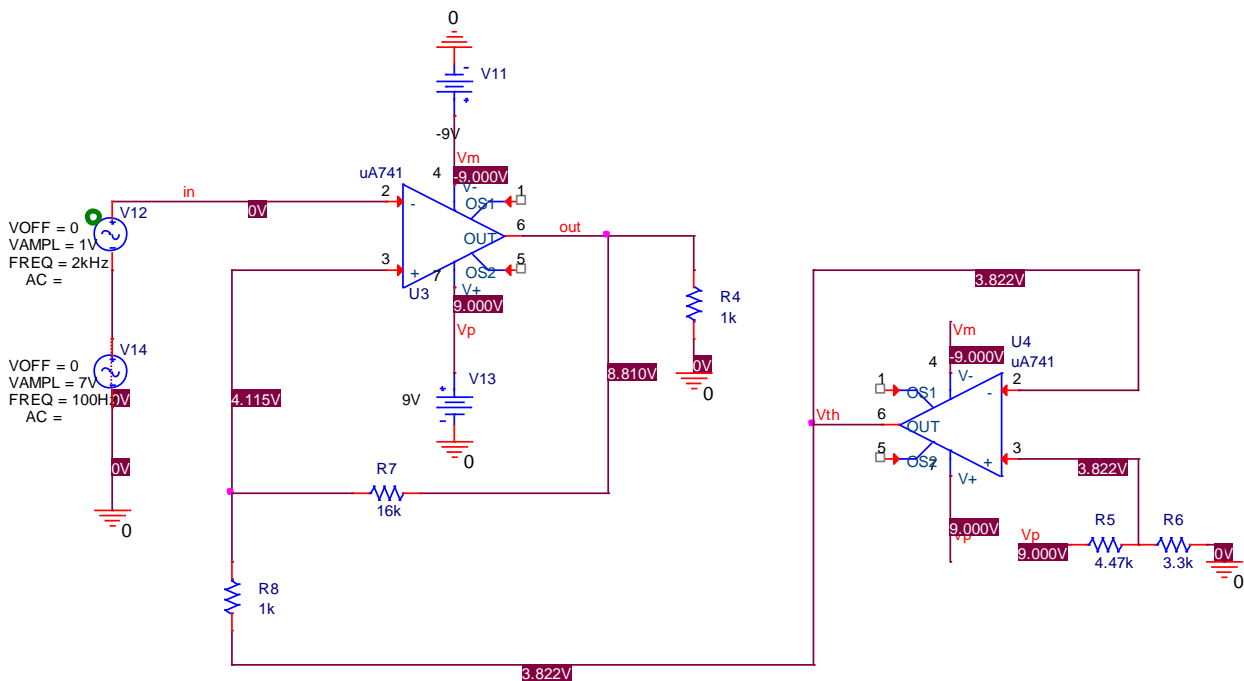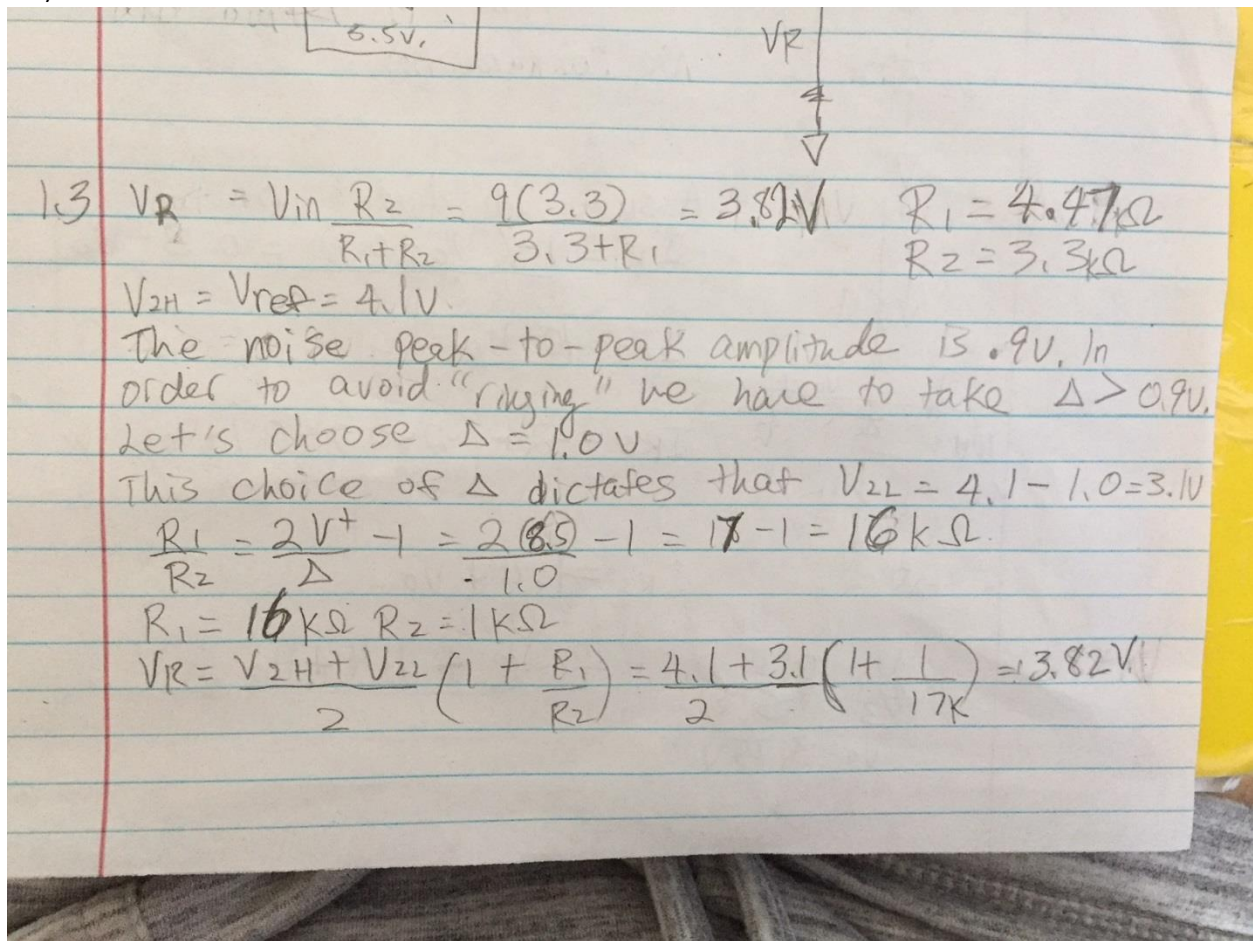


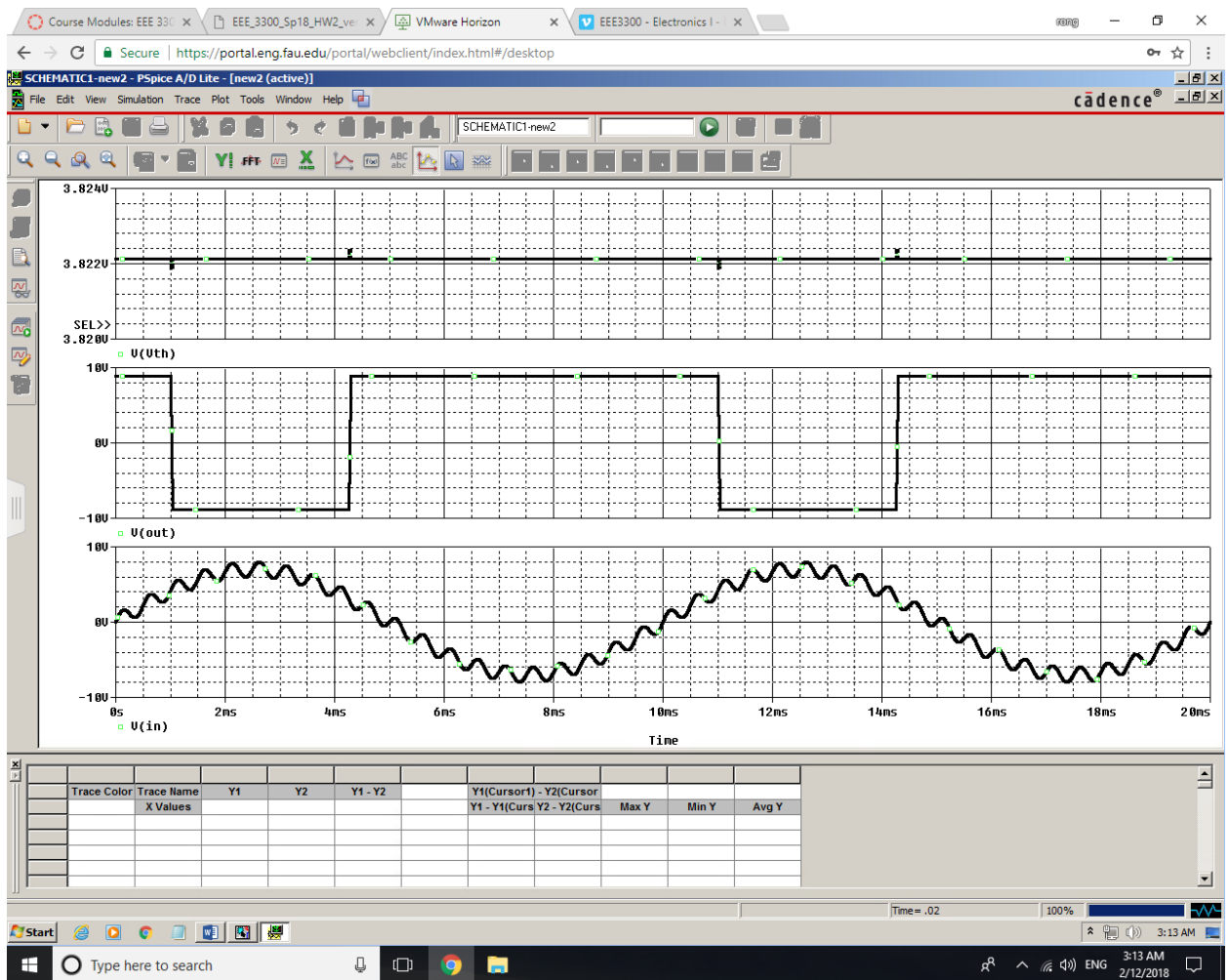

2.1)

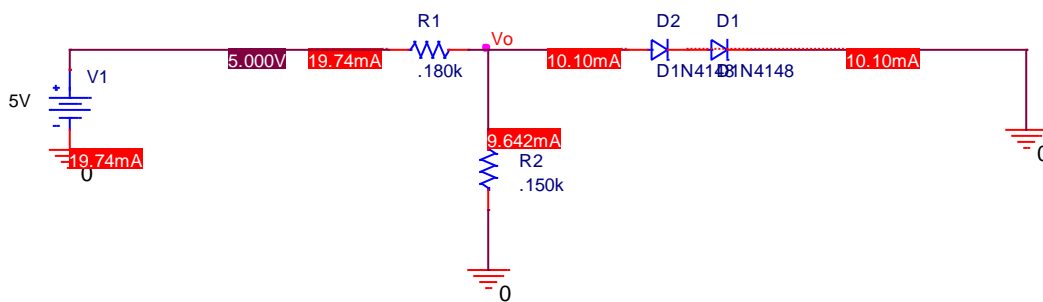2.1) Assume diodes on $2V_D = V_o = 1.4$ $V_D = V_o = 0.7$
 $i = \frac{5 - V_o}{R} = \frac{5 - 1.4}{180k\Omega} = 20mA$ $V_D = 5 - 0.7 = 4.3$ $24mA$
 Assume diodes off, $V_D = V_o = 5V$
 There is a contradiction because the current is 0, between 5 volt and ground there's diodes that are off, doesn't make sense.
 $V_o = 0V$
 2.2) The diodes are on. $V_o = 2V_D = 1.4$
 $i = \frac{5 - V_o}{R} = \frac{5 - 1.4}{1k\Omega} = 3.6mA$
 2.3) Assume diodes on. $V_o = 2.5V$



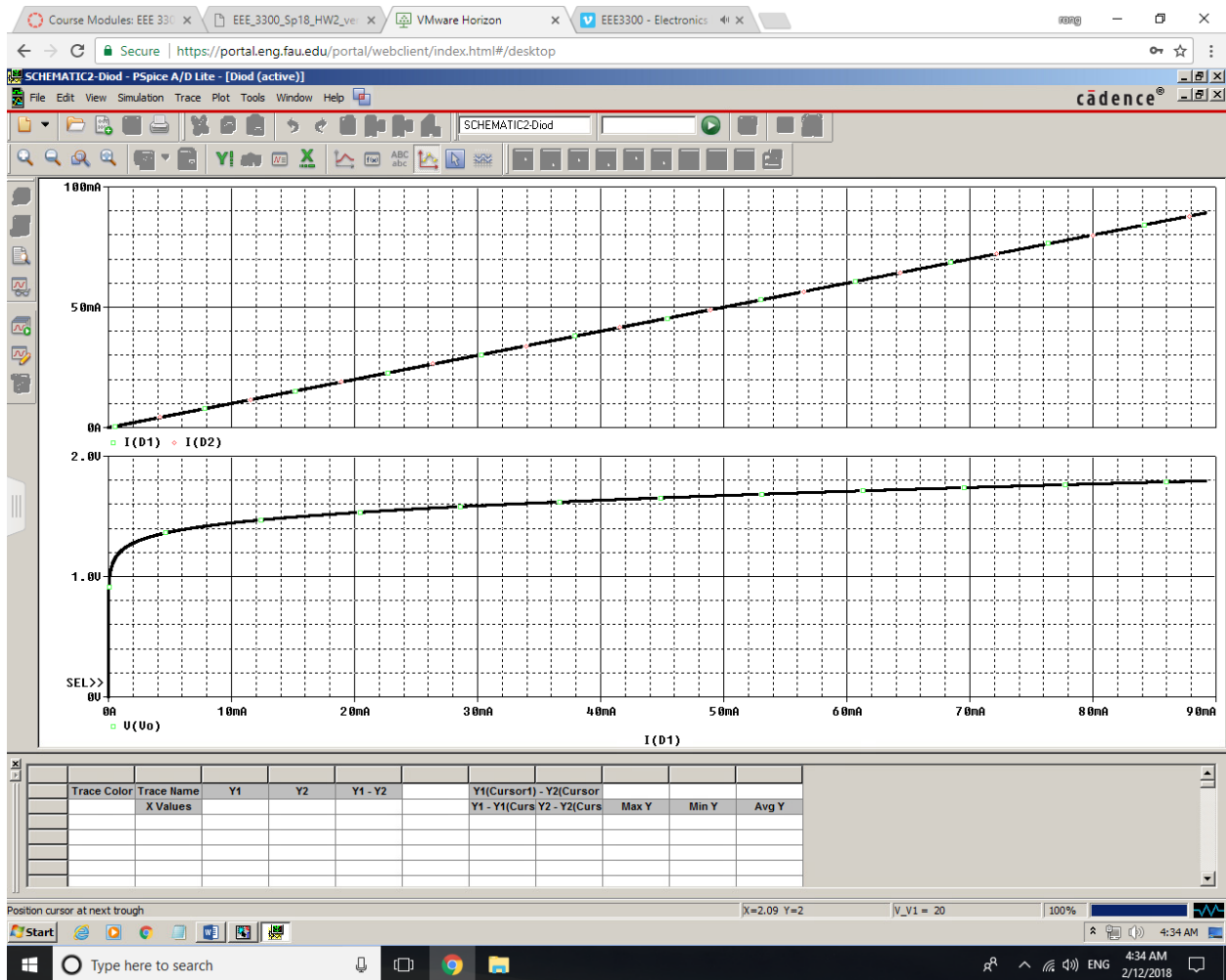

2.2)

2.1) Assume diodes on. $V_D = V_0 = 1.4$. $V_D = V_0$

$$i = \frac{5 - V_0}{R} = \frac{5 - 1.4}{180k} = 20\mu A$$


 Assume diodes off. $V_D = V_0 = 5V$
 There is a contradiction because there is 0V between 5 volt and ground that are off, doesn't make sense.
 $V_0 = 0V$
 2.2) The diodes are on. $V_0 = 2V_D = 1.4$


$$i = \frac{5 - V_0}{R} = \frac{5 - 1.4}{1k} = 3.6mA$$

 2.3) Assume diodes on.
 $0.7 + 1.8 = 2.5V$

$$i = \frac{5 - 2.5}{180} = 14\mu A$$

 No contradiction.

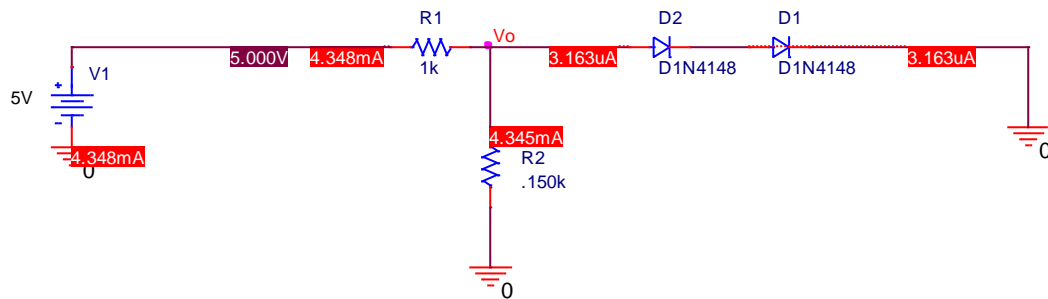

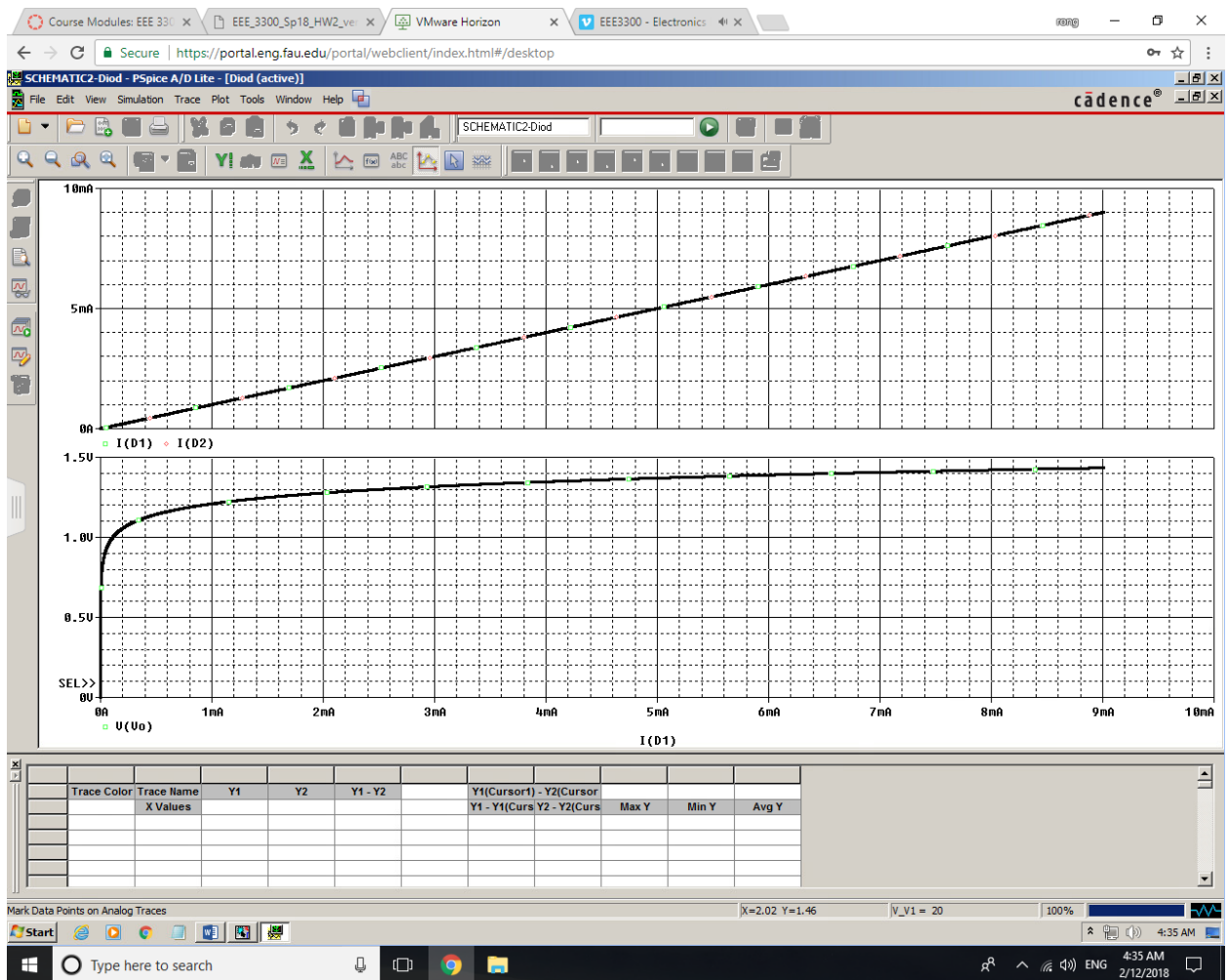

2.3)


is 0, between 5 volt and ground there's that are off, doesn't make sense.

$V_o = 0V$

2.2) The diodes are on. $V_o = 2V_o = 1.4$
 $I = \frac{5 - V_o}{R} = \frac{5 - 1.4}{1k\Omega} = 3.6mA$

2.3) Assume diodes on.
 $0.7 + 1.8 = 2.5V$
 $I = \frac{5 - 2.5}{1.8k\Omega} = 1.4mA$
 No contradiction.

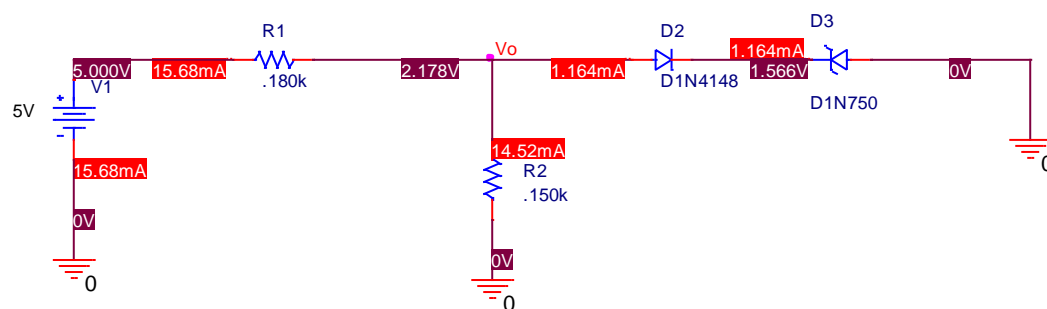
2.4) Assume all diodes on.
 $I_{R1} = \frac{5 - (V_o + 0.7)}{1k\Omega} = 0.3 - V_o$
 $I_{R2} = \frac{V_o}{1.5k\Omega}$





2.4)

2.4)

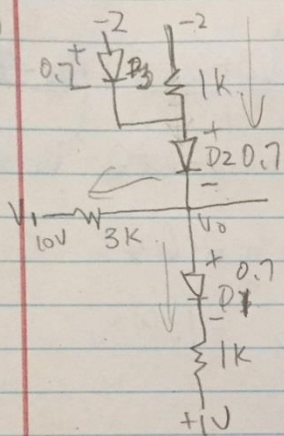


Assume D_1 on, D_2 and D_3 off

$$\frac{V_0 - 10}{3} + \frac{(V_0 + 0.7 - 1)}{1} = 0$$

$$\frac{4}{3}V_0 - 3.63 = 0$$

$$V_0 = 2.725 \text{ V}$$

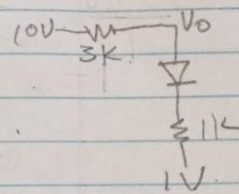


Assume D_1 on, D_2 on, D_3 off

$$\frac{(V_0 + 0.7) - (-2)}{1} + \frac{V_0 - 10}{3} + \frac{(V_0 + 0.7 - 1)}{1} = 0$$


$$V_0 + 2.7 + \frac{V_0}{3} - \frac{10}{3} + V_0 - 0.3 = 0$$


$$\frac{7}{3}V_0 - 0.9333 = 0$$

$$V_0 = 0.4 \text{ V}$$

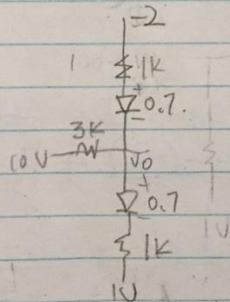

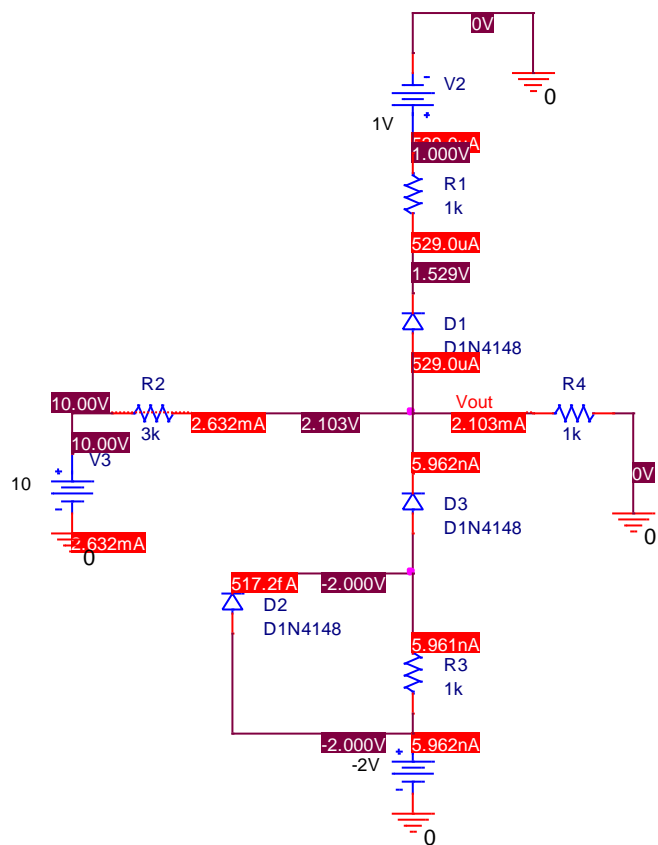
The voltage across $D_3 = +2 - 0.7 = -2.7 \text{ V}$. The voltage across D_2 is $= 2 - (-2.7) = 4.7 \text{ V}$ which justifies the assumption D_2 is on. D_3 and D_1 also has to be on.



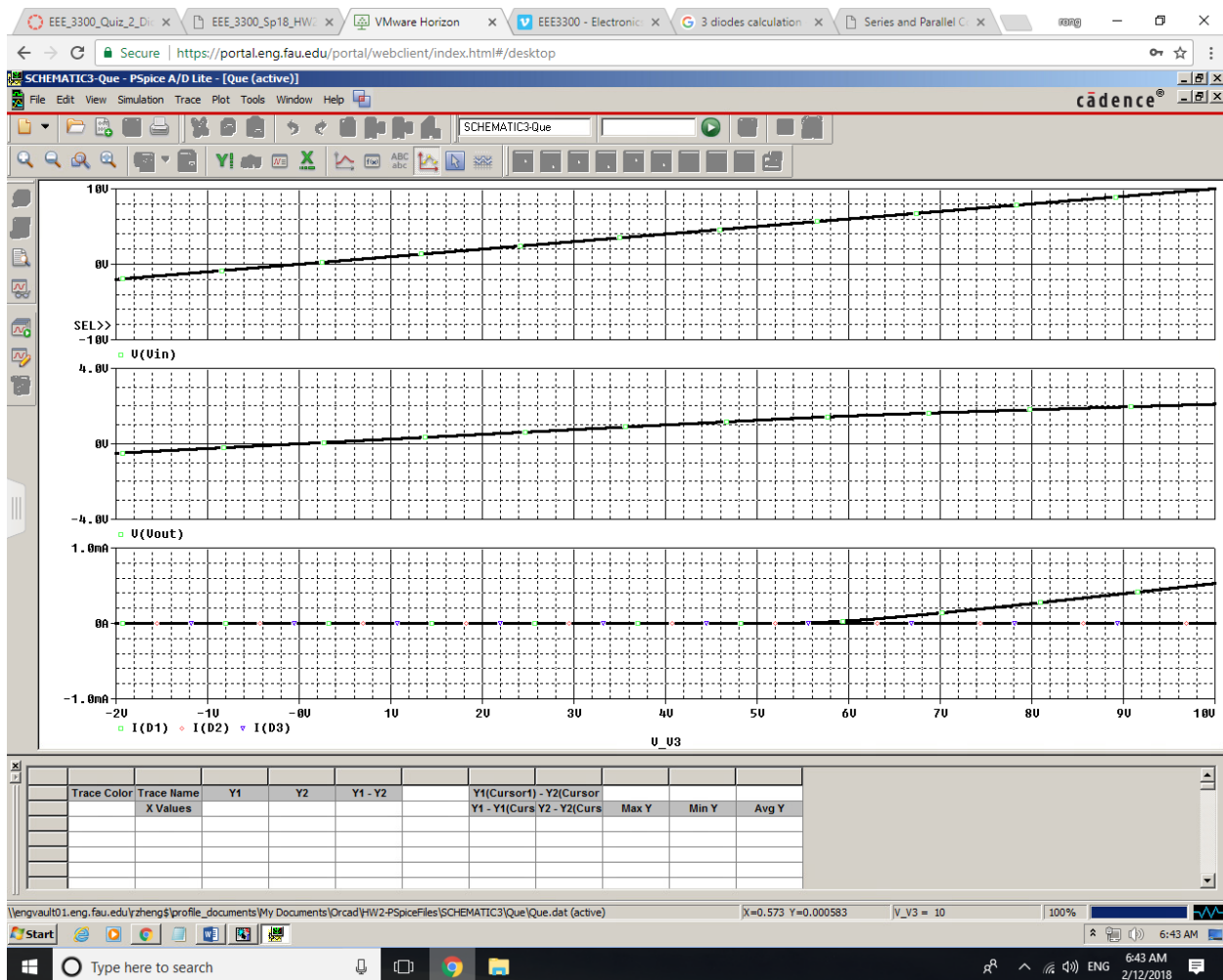



2.5)

2.5) Assume D_1 , D_2 , D_3 all on.

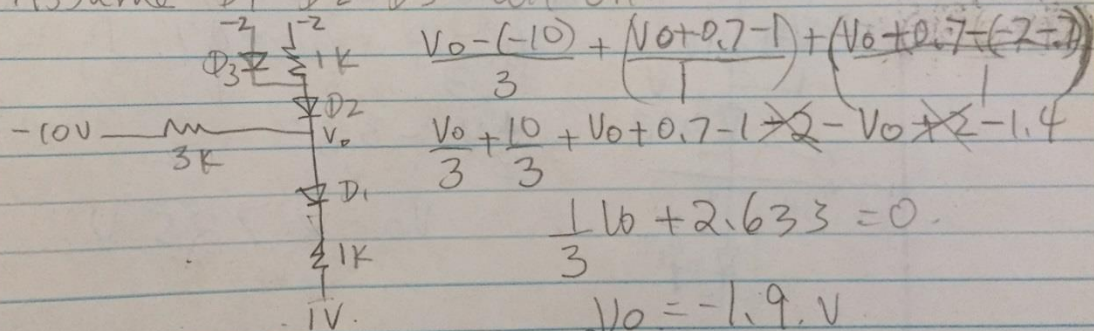

D_1 on, D_2 and D_3 off.

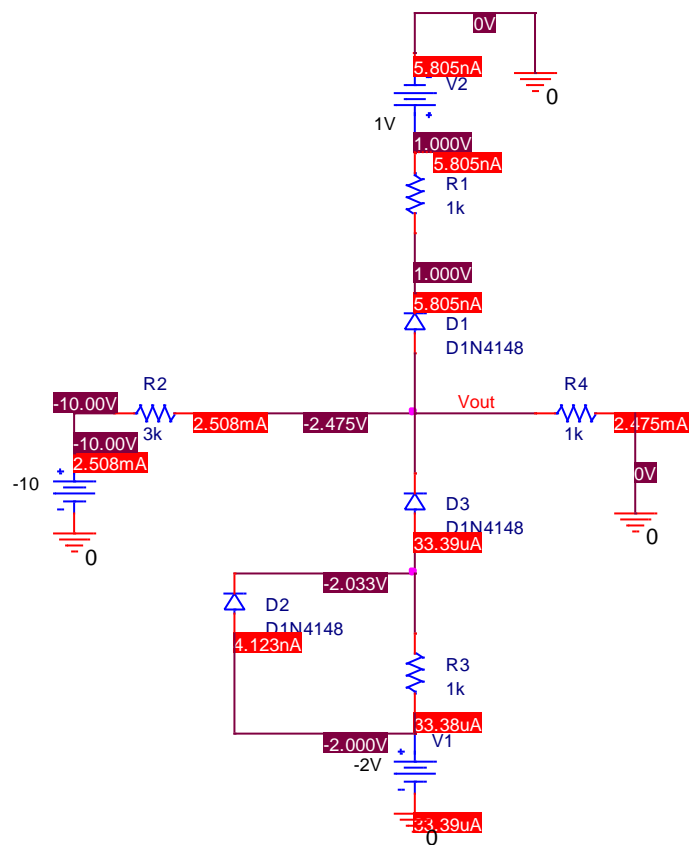


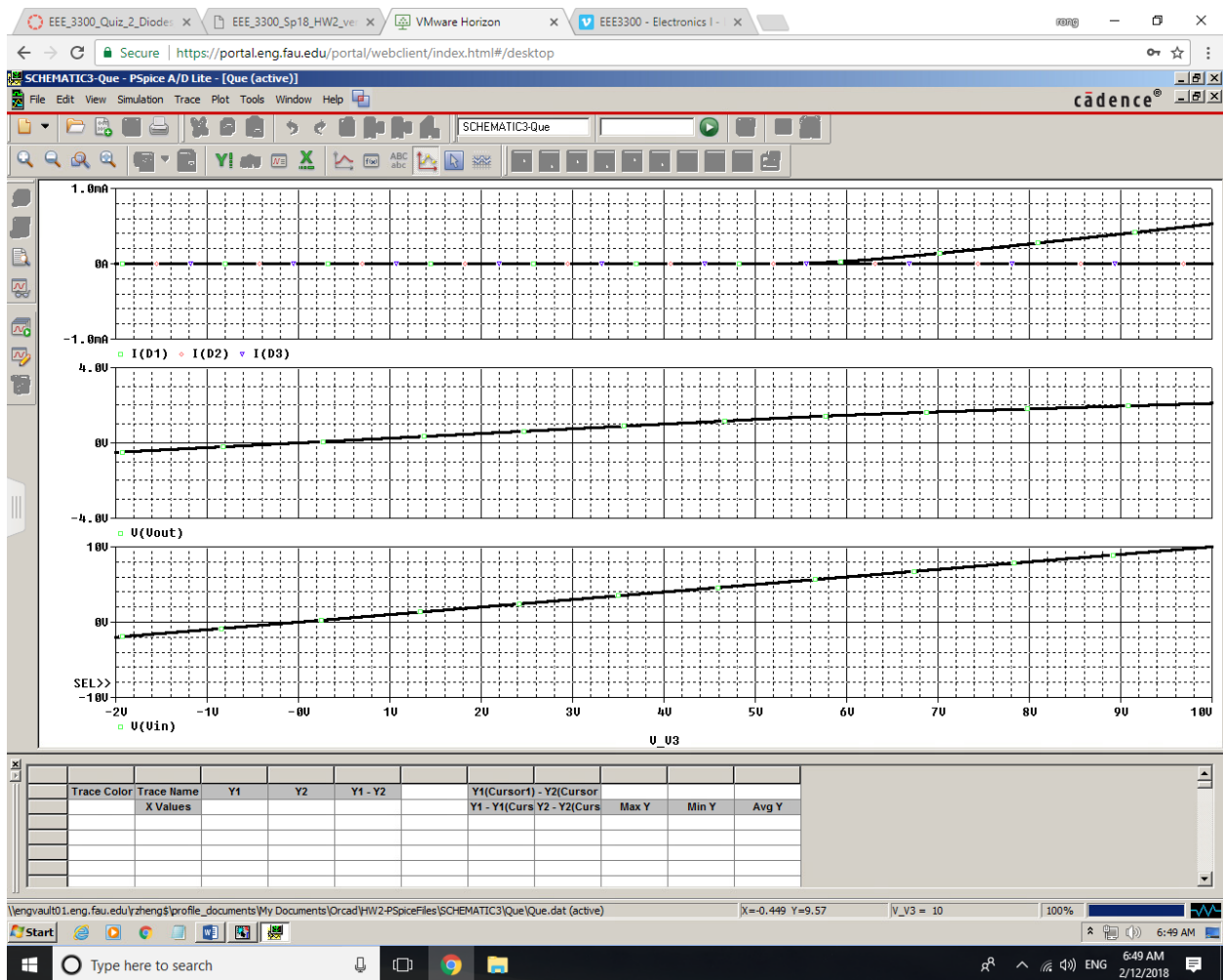

2.6)

D_1 on, D_2 and D_3 off.

2.6) Assume D_1 on, D_2 on, D_3 off.

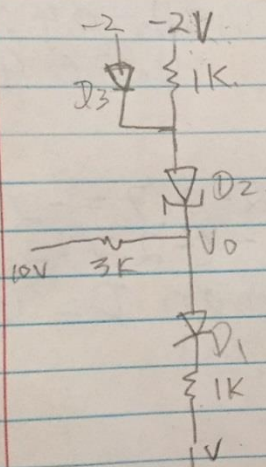

$$\frac{V_0 + D_2 - (-2)}{1} + \frac{V_0 - 10}{3} + \frac{(V_0 + D_1 - 1)}{1} = 0$$

$$\frac{V_0 + 5.1 + 2}{1} + \frac{V_0 - 10}{3} + \frac{V_0 + 0.7 - 1}{1} = 0$$

$$\frac{7}{3} V_0 + 3.4667 = 0$$

$$V_0 = -1.485 V$$

D_3 off, D_2 on, D_1 on

